

Columbia University
Department of Electrical Engineering
EECS E4340. Laboratory #4A.
PDP-8 Execution Controls, Part II. I/O Interface.
Due: April 7, 2004

In this laboratory, you will complete the VHDL for your PDP/8 design by implementing the the execution controls for the IOT instruction and the interface to the 16550 UART. Please use the design we discussed in class as a starting point. The I/O interface to the UART should have the following entity:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY uart_interface IS
    PORT(
        acclr : OUT std_ulogic;
        ioskip : OUT std_ulogic;
        orac : OUT std_ulogic;
        uart_address : OUT std_ulogic_vector(0 TO 2);
        uart_cs0 : OUT std_ulogic;
        uart_read : OUT std_ulogic;
        uart_write : OUT std_ulogic;
        int_request : OUT std_ulogic;
        iop1 : IN std_ulogic;
        iop2 : IN std_ulogic;
        iop4 : IN std_ulogic;
        iop_device_address : IN std_ulogic_vector(0 TO 4);
        rxrdy_bar : IN std_ulogic;
        txrdy_bar : IN std_ulogic
    );
END uart_interface;
```

You will need to complete the ASM charts for the execution cycles of the IOT instructions.

Since we do not have a VHDL behavioral for the UART (it is actually quite difficult to get this right), you will do most of your testing in hardware. Do try executing a “polling” loop for TTY input and output and make sure

“sensible” commands are being send to the UART. You may want to use your testbench to toggle `rxrdy_bar` and `txrdy_bar`.

Please turn in your VHDL, the ASM charts for your controller, your testbench, and detailed description of your testing including any relevant waveform plots.