

Columbia University  
Department of Electrical Engineering  
EECS E4340. VHDL examples.

**Basic example**

We will use the `std_ulogic` and `std_ulogic_vector` types defined in the `ieee.std_logic_1164` package. You have access to basic logic operators.

```
library ieee;
use ieee.std_logic_1164.all;
entity full_adder is
    port(a, b, cin: in std_ulogic;
         sum, cout: out std_ulogic);
end full_adder;
architecture dataflow of full_adder is
begin
    sum <= (a xor b) xor c;
    carry <= (a and b) or (a and c) or (b and c);
end dataflow;
```

**Other concurrent VHDL statements**

when . . . else is a useful concurrent VHDL statement.

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_1 is
    port(in0, in1, in2, in3: in std_ulogic_vector(0 to 15);
         s0, s1: in std_ulogic;
         z: out std_ulogic_vector(0 to 15));
end multiplexer_4_1;
architecture dataflow of multiplexer_4_1 is
begin
    z <= in0 when (s0 = '0' and s1 = '0') else
        in1 when (s0 = '1' and s1 = '0') else
        in2 when (s0 = '0' and s1 = '1') else
        in3 when (s0 = '1' and s1 = '1') else
        "XXXXXXXXXXXXXXXXXX";
end dataflow;
```

## Here's another way of doing the multiplexer

with . . . select is also useful.

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_1 is
  port(in0, in1, in2, in3: in std_ulogic_vector(0 to 15);
        s0, s1: in std_ulogic;
        z: out std_ulogic_vector(0 to 15));
end multiplexer_4_1;
architecture dataflow of multiplexer_4_1 is
  signal sels: std_ulogic_vector(0 to 1);
begin
  sels <= s0 & s1;
  with sels select
    z <= in0 when "00",
         in1 when "01",
         in2 when "10",
         in3 when "11",
         "XXXXXXXXXXXXXXXX" when others;
end dataflow;
```

## But maybe the selects cannot both be 1 or 0

Use can use VHDL assert statements to flag invalid conditions.

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_2_1 is
  port(in0, in1: in std_ulogic_vector(0 to 15);
        s0, s1: in std_ulogic;
        z: out std_ulogic_vector(0 to 15));
end multiplexer_2_1;
architecture dataflow of multiplexer_2_1 is
  signal sels: std_ulogic_vector(0 to 1);
begin
  sels <= s0 & s1;
  with sels select
```

```

    z <= in0 when "10",
        in1 when "01",
        "XXXXXXXXXXXXXXXX" when others;
assert not(sels = "00" or sels = "11")
    report "The select signals must be orthogonal!"
    severity ERROR;
end dataflow;

```

### Tristate drivers

Note the use of the resolved `std_logic` type on signal `z`.

```

library ieee;
use ieee.std_logic_1164.all;
entity part1 is
    port(a, sel: in std_ulogic;
        z: out std_logic);
end part1;
architecture dataflow of part1 is
begin
    z <= a when (sel = '1') else 'Z';
end dataflow;

```

### 4-bit adder with concurrent VHDL

```

library ieee;
use ieee.std_logic_1164.all;
entity adder is
    port(a, b: in std_ulogic_vector(0 to 3);
        cin: in std_ulogic;
        sum: out std_ulogic_vector(0 to 3);
        cout: out std_ulogic);
end adder;
architecture dataflow of adder is
signal car: std_ulogic_vector(0 to 4);
begin
    car(0) <= cin;
    G1: for m in 3 downto 0 generate

```

```

    sum(m) <= a(m) xor b(m) xor car(m);
    car(m+1) <= (a(m) and b(m)) or (b(m) and car(m)) or (a(m) and car(m));
end generate G1;
cout <= car(4);
end dataflow;

```

### 16-bit carry-lookahead adder

Coding at this level of detail ensures that the adder is logically structured exactly the way you want it.

```

library ieee;
use ieee.std_logic_1164.all;
entity adder_16 is
    port(a, b: in std_ulogic_vector(0 to 15);
          sum: out std_ulogic_vector(0 to 15);
          cout: out std_ulogic);
end adder_16;
architecture dataflow of adder_16 is
    signal car: std_ulogic_vector(0 to 16);
    signal pg, gg: std_ulogic_vector(0 to 3);
begin
    -- full adder blocks
    G1: for m in 0 to 15 generate
        sum(m) <= p(m) xor g(m) xor car(m);
        g(m) <= a(m) and b(m);
        p(m) <= a(m) or b(m);
    end generate G1;
    G2: for m in 0 to 3 generate
        gg(m) <= g(4*m+3) or (p(4*m+3) and g(4*m+2)) or
            (p(4*m+3) and p(4*m+2) and g(4*m+1)) or
            (p(4*m+3) and p(4*m+2) and p(4*m+1) and g(4*m));
        pg(m) <= p(4*m+3) and p(4*m+2) and p(4*m+1) and p(4*m));
        car(4*m+1) <= g(4*m) or (p(4*m) and car(4*m));
        car(4*m+2) <= g(4*m+1) or (p(4*m+1) and g(4*m)) or
            (p(4*m+1) and p(4*m) and car(4*m));
        car(4*m+3) <= g(4*m+2) or (p(4*m+2) and g(4*m+1)) or
            (p(4*m+2) and p(4*m+1) and g(4*m)) or

```

```

                (p(4*m+2) and p(4*m+1) and p(4*m) and car(4*m));
end generate G2;
car(0) <= cin;
car(4) <= gg(0) or (pg(0) and car(0));
car(8) <= gg(1) or (pg(1) and gg(0)) or
        (pg(1) and pg(0) and car(0));
car(12) <= gg(2) or (pg(2) and gg(1)) or
        (pg(2) and pg(1) and gg(0)) or
        (pg(2) and pg(1) and pg(0) and car(0));
car(16) <= gg(3) or (pg(3) and gg(2)) or
        (pg(3) and pg(2) and gg(1)) or
        (pg(3) and pg(2) and pg(1) and gg(0)) or
        (pg(3) and pg(2) and pg(1) and pg(0) and car(0));
cout <= car(16);
end dataflow;

```

#### 4-bit adder using the std\_logic\_arith package

In this case, we use a “higher-level” arithmetic operator. In general, you must be very careful when you do this because you lose control over the detailed logic implementation of the adder (in this case). The synthesis tool will implement this a certain way (for example, a ripple-carry adder) which might not be acceptable for a particular application.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_
use ieee.std_logic_arith.all;
entity adder is
    port(a, b: in std_ulogic_vector(0 to 3);
         cin: in std_ulogic;
         c: out std_ulogic_vector(0 to 3);
         cout: out std_ulogic);
end adder;
architecture dataflow of adder is
    signal temp_sum: std_ulogic_vector(0 to 4);
begin
    temp_sum <= to_stdulogicvector((unsigned(a) + unsigned(b))

```

```

        + conv_unsigned(cin,1));
    cout <= temp_sum(0);
    c <= temp_sum(1 to 4);
end dataflow;

```

### Positive edge-trigger 32-bit register

VHDL process statements are the preferred mechanism for defining flip-flops and registers.

```

library ieee;
use ieee.std_logic_1164.all;
entity register_32 is
    port(clk, write_enable: in std_ulogic;
         data_in: in std_ulogic_vector(0 to 31);
         data_out: out std_ulogic_vector(0 to 31));
end register_32;
architecture dataflow of register_32 is
begin
    process(clk)
    begin
        if ((clk = '1') and not(clk'stable) and (write_enable = '1')) then
            data_out <= data_in;
        end if;
    end process;
end dataflow;

```

### 8-bit right shifter

Note the use of the concatenation operator & to form the shifter.

```

library ieee;
use ieee.std_logic_1164.all;
entity eight_bit_shifter is
    port(shift_in: in std_ulogic_vector(0 to 7);
         shift_out: out std_ulogic_vector(0 to 7);
         shift_control: in std_ulogic_vector(0 to 2));
end eight_bit_shifter;
architecture dataflow of eight_bit_shifter is

```

```

signal first_stage: std_ulogic_vector(0 to 7);
signal second_stage: std_ulogic_vector(0 to 7);
begin
  first_stage <= shift_in when (shift_control(0) = '0') else
    ("0" & shift_in(0 to 6));
  second_stage <= first_stage when (shift_control(0) = '0') else
    ("00" & first_stage(0 to 5));
  shift_out <= second_stage when (shift_control(2) = '0') else
    ("0000" & second_stage(0 to 4));
end dataflow;

```

### Dataflow example. Counter in traffic light problem.

Note how this matches precisely the “block-diagram” structure of the design that we discussed in class. VHDL should be used to capture logic design; it should not be used as a programming language.

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.std_logic_arith.all;
ENTITY counter IS
  PORT(
    long : OUT std_ulogic;
    short : OUT std_ulogic;
    start_timer : IN std_ulogic;
    clock : IN std_ulogic
  );
END counter;
architecture dataflow of counter is
  signal latch_in, latch_out, incr_out: std_ulogic_vector(0 to 6);
  signal short_int, long_int, short_temp, long_temp: std_ulogic;
begin
  sync: process(clock)
  begin
    if (clock = '1' and not(clock'stable)) then
      latch_out <= latch_in;
      short_temp <= not(start_timer) and (short_int or short_temp);

```

```

        long_temp <= not(start_timer) and (long_int or long_temp);
    end if;
end process;
latch_in <= "0000000" when (start_timer = '1') else incr_out;
incr_out <= to_stdulogicvector(unsigned(latch_out) + '1');
short_int <= '1' when (incr_out = "0100000") else
    '0';
long_int <= '1' when (incr_out = "1000000") else
    '0';

short <= short_temp;
long <= long_temp;
end dataflow;

```

### ASM translation to VHDL. Traffic light controller.

ASM's can be translated to VHDL in a completely formulaic manner. One process is used for the state register. Another process can be used for the combinational logic of the state machine. This second process must be combinational. To ensure this, two conditions must be satisfied:

- The process must be activated by all inputs of the combinational logic block.
- All "cases" must be covered in the logic.

Note the use of VHDL constants to define the states. This makes the code easier to read and makes the state encodings easy to change.

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY controller IS
    PORT(
        h11 : OUT std_ulogic;
        h10 : OUT std_ulogic;
        f11 : OUT std_ulogic;
        f10 : OUT std_ulogic;
        start_timer : OUT std_ulogic;
        clock : IN std_ulogic;

```

```

        reset : IN std_ulogic;
        cars : IN std_ulogic;
        short : IN std_ulogic;
        long : IN std_ulogic
    );
END controller;
architecture behavior of controller is

    signal current_state, next_state: std_ulogic_vector(0 to 1);
    constant HG: std_ulogic_vector := "00";
    constant HY: std_ulogic_vector := "01";
    constant FY: std_ulogic_vector := "10";
    constant FG: std_ulogic_vector := "11";

begin

    sync: process(clock)
    begin
        if ((clock = '1') and not(clock'stable)) then
            current_state <= next_state;
        end if;
    end process sync;

    fsm_comb: process(current_state, short, long, cars)
    begin
        next_state <= current_state;
        h11 <= '0';
        h10 <= '0';
        f11 <= '0';
        f10 <= '0';
        start_time <= '0';
        if (reset = '1') then -- synchronous reset
            next_state <= HG;
            start_timer <= '1';
        else
            case current_state is
                when HG =>

```

```

-- set lights
h11 <= '0';
h10 <= '0';
f11 <= '0';
f10 <= '1';
if (cars and long) = '1' then
    next_state <= HY;
    start_timer <= '1';
else
    next_state <= HG;
end if;
when HY =>
    -- set lights
    h11 <= '1';
    h10 <= '0';
    f11 <= '0';
    f10 <= '1';
    if short = '1' then
        next_state <= FG;
        start_timer <= '1';
    else
        next_state <= HY;
    end if;
when FG =>
    h11 <= '0';
    h10 <= '1';
    f11 <= '0';
    f10 <= '0';
    if (not(cars) or long) = '1' then
        next_state <= FY;
        start_timer <= '1';
    else
        next_state <= FG;
    end if;
when FY =>
    h11 <= '0';
    h10 <= '1';

```

```

        fl1 <= '1';
        fl0 <= '0';
        if (short = '1') then
            next_state <= HG;
            start_timer <= '1';
        else
            next_state <= FY;
        end if;
    when others =>
        next_state <= "XX";
        start_timer <= 'X';
        h10 <= 'X';
        h11 <= 'X';
        f10 <= 'X';
        f11 <= 'X';
    end case;
end if;
end process;
end behavior;

```

**You can make a latch you don't intend if you aren't careful with processes**

In this case, I violated the second rule for a “combinational” process and did not cover all cases.

```

library ieee;
use ieee.std_logic_1164.all;
entity is_latch is
    port(a: in std_ulogic;
         b: out std_ulogic);
end is_latch;
architecture dataflow of is_latch is
begin
    process(a)
    begin
        if (a = '0') then
            b <= '1';
        end if;
    end process;
end architecture;

```

```

        end if;
    end process;
end dataflow;

```

### Modelling an SRAM. Use of variables.

Memory modelling is really the only legitimate use of VHDL variables in RTL design.

```

library ieee;
use ieee.std_logic_1164.all;
entity sram_2168 is
    port( io: inout std_logic_vector(0 to 3);
          addr: in std_ulogic_vector(0 to 11);
          ce_n: in std_ulogic;
          we_n: in std_ulogic);
end sram_2168;
architecture dataflow of sram_2168 is
begin
    memory: process(addr, ce_n, we_n)
        type sram_array_word is std_ulogic_vector(0 to 3);
        variable sram_array: array(0 to 4096) of sram_array_word;
    begin
        if (ce_n = '0') then
            if (we_n = '1') then -- read the memory
                io <= sram_array(to_integer(addr));
            else
                sram_array(to_integer(addr)) := io;
            end if;
        else
            io <= "ZZZZ";
        end if;
    end process;
end dataflow;

```

### There is a difference between signals and variables in processes

These examples indicate the subtle difference between signals and variables in processes.

```

entity what_is_b is
end what_is_b;
architecture dataflow of what_is_b is
signal a, b: std_ulogic;
begin
  process
  begin
    a <= '1';
    if (a = '1') then
      b <= '1';
    else
      b <= '0';
    end if;
  end process;
end dataflow;'

```

```

entity what_is_b is
end what_is_b;
architecture dataflow of what_is_b is
signal b: std_ulogic;
begin
  process
  variable a: std_ulogic;
  begin
    a := '1';
    if (a = '1') then
      b <= '1';
    else
      b <= '0';
    end if;
  end process;
end dataflow;'

```

### **Testbench example**

Testbenches are how you supply a stimulus to your design.1

ENTITY test IS

```

END test;
LIBRARY ieee, light;
USE ieee.std_logic_1164.all;
ARCHITECTURE stimulus OF test IS

    COMPONENT traffic_light
        PORT(
            h10 : OUT std_ulogic;
            h11 : OUT std_ulogic;
            f10 : OUT std_ulogic;
            f11 : OUT std_ulogic;
            clock : IN std_ulogic;
            reset : IN std_ulogic;
            cars : IN std_ulogic
        );
    END COMPONENT;

    -- Fill in values for each generic

    -- Fill in values for each signal
    SIGNAL h10 : std_ulogic;
    SIGNAL h11 : std_ulogic;
    SIGNAL f10 : std_ulogic;
    SIGNAL f11 : std_ulogic;
    SIGNAL clock : std_ulogic := '0';
    SIGNAL reset : std_ulogic := '1';
    SIGNAL cars : std_ulogic;

    FOR ALL: traffic_light USE ENTITY light.traffic_light(schematic);

BEGIN

    dut : traffic_light

        PORT MAP (h10, h11, f10, f11, clock, reset, cars);

    reset <= '1', '0' after 1 ms;

```

```

    clock <= not(clock) after 50 ms;
    cars <= '0', '1' after 200 ms, '0' after 700 ms,
          '1' after 1200 ms, '0' after 7200 ms, '1' after 7300 ms,
          '0' after 17300 ms;
END stimulus;

```

### Testbench example using a process for waveform generation

```

ENTITY test IS
END test;
LIBRARY ieee, light;
USE ieee.std_logic_1164.all;
ARCHITECTURE stimulus OF test IS

    COMPONENT traffic_light
        PORT(
            h10 : OUT std_ulogic;
            h11 : OUT std_ulogic;
            f10 : OUT std_ulogic;
            f11 : OUT std_ulogic;
            clock : IN std_ulogic;
            reset : IN std_ulogic;
            cars : IN std_ulogic
        );
    END COMPONENT;

    -- Fill in values for each generic

    -- Fill in values for each signal
    SIGNAL h10 : std_ulogic;
    SIGNAL h11 : std_ulogic;
    SIGNAL f10 : std_ulogic;
    SIGNAL f11 : std_ulogic;
    SIGNAL clock : std_ulogic := '0';
    SIGNAL reset : std_ulogic := '1';
    SIGNAL cars : std_ulogic;

```

```

FOR ALL: traffic_light USE ENTITY light.traffic_light(schematic);

BEGIN

    dut : traffic_light

        PORT MAP (h10, h11, f10, f11, clock, reset, cars);

    reset <= '1', '0' after 1 ms;
    clock <= not(clock) after 50 ms;

    process
    begin
        cars <= '0';

        wait for 200 ms;
        cars <= '1';

        wait for 500 ms;
        cars <= '0';

        wait for 500 ms;
        cars <= '1';

        wait for 5000 ms;
        cars <= '0';

        wait for 100 ms;
        cars <= '1';

        wait for 10000 ms;
        cars <= '0';
    end process;

END stimulus;

```