

# E4215: Analog Filter Synthesis and Design: HW2

Nagendra Krishnapura (nkrishnapura@mltc.com)

due on 4 Feb. 2003

For the opamps, use the appropriate model based on the parameters provided. i.e. if nothing is given, assume an ideal opamp with infinite gain; if the unity gain frequency is given, use the integrator model; if the dc gain and the unity gain frequency are given, use the first order model etc. This holds for all future assignments.

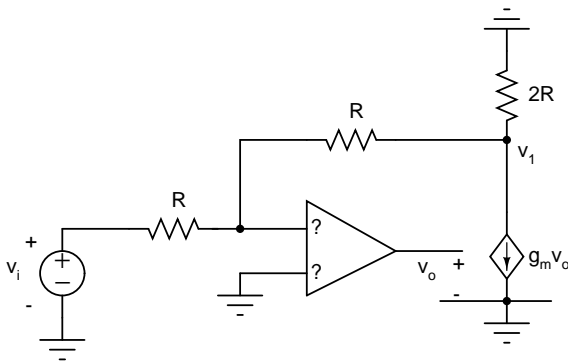


Figure 1:

1. (2 pts.) [Fig. 1,  $g_m = 4/R$ ] Assign the correct signs to the opamp such that it has negative feedback at dc.
2. (2 pts.) [Fig. 1,  $g_m = 4/R$ ] Assuming that the opamp has a transfer function  $A(s) = \omega_u/s$ , determine the transfer functions  $V_o(s)/V_i(s)$ ,  $V_1(s)/V_i(s)$ .
3. (4 pts.) [Fig. 1,  $g_m = 4/R$ ] Determine the loop gain  $T(s)$  around this feedback loop. Assuming that the opamp has a dc gain  $A_o = 100$  and a

unity gain frequency  $\omega_u = 1 \text{ Grad/s}^1$ , draw the Bode plot (magnitude and phase) of loop gain  $T(s)$  and op amp gain  $A(s)$ .

4. (6 pts.) Assume  $g_m = 1 \text{ mS}$ ,  $R_1 = 900 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $R_L = \infty$ ,  $A_o = 1000$ . For the circuits in Fig. 2(a) and Fig. 2(b), evaluate the gain  $V_o/V_i$  and the feedback loop gain T. Repeat, assuming  $R_L = 1 \text{ M}\Omega$ .
5. (6 pts.) Assume  $g_m = 1 \text{ mS}$ ,  $R_1 = 900 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $C_L = 10 \text{ pF}$ ,  $A_o = 1000$ ,  $\omega_u = 100 \text{ Mrad/s}^2$ . For the circuits in Fig. 2(c) and Fig. 2(d), evaluate the transfer function  $V_o(s)/V_i(s)$  and the feedback loop gain T(s). Write the transfer functions in the standard first order form and compare the two results. Repeat, assuming  $C_L = 20 \text{ pF}$ .

<sup>1</sup>giga radians/second; giga= $10^9$   
<sup>2</sup>mega radians/second

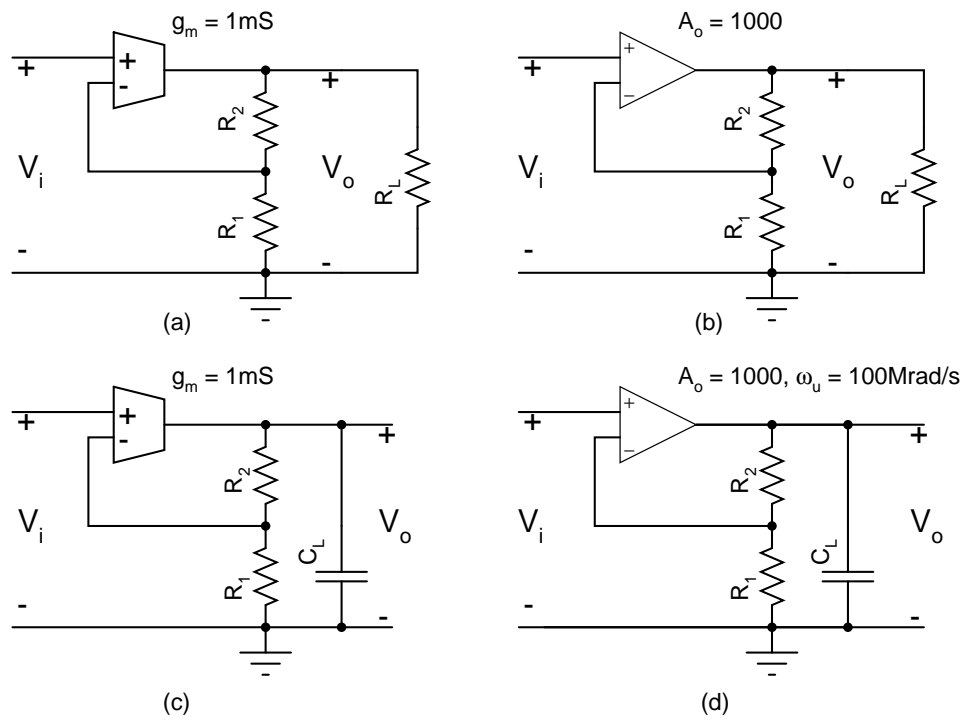


Figure 2: