

E4215: Analog Filter Synthesis and Design: HW6

Nagendra Krishnapura (nkrishnapura@mltc.com)

due on 4 Mar. 2003

In addition to the problems here, problem #5 from HW5 is also due on 4 Mar. 2003

- (1+3+3 pts.) Repeat the design in problem #5 of HW5 using opamps and *feedforward* technique. Use 10 pF capacitors.
 - Design the Butterworth lowpass filter.
 - Obtain the lowpass notch transfer function at the output V_1 ¹.
 - Obtain the lowpass notch transfer function at the output V_2 .

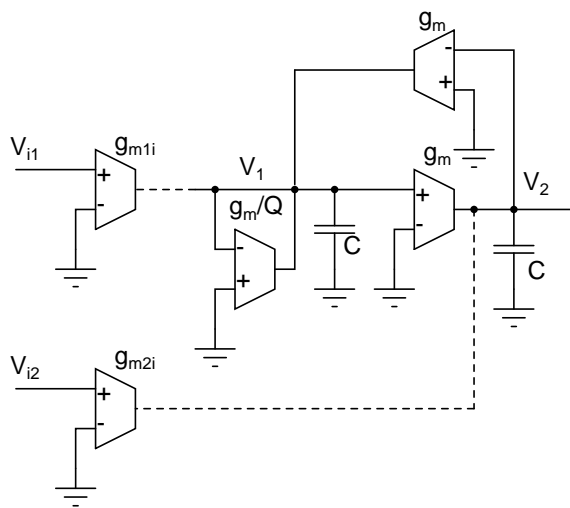


Figure 1:

- (2 pts.) In Fig. 1, Determine the transfer functions from V_{i1} and V_{i2} to voltages V_1 and V_2 .

¹output of OPA1; in the handout “Transfer functions realizable in a biquad”.

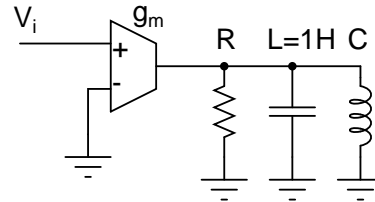


Figure 2:

- (1+2+2+2+1+3 pts.)
 - Design a 1 H inductor using transconductors and a 100 pF capacitor.
 - Derive the (passive) equivalent circuit of the previously designed inductor if the capacitor had a 1 M Ω resistor across it.
 - Design an RLC bandpass filter with $\omega_p = 100$ krad/s and $Q = 10$ using a 1 H inductor. The gain at the resonant frequency should be 10. Use the topology in Fig. 2.
 - Replace the inductor with the equivalent circuit obtained in (b) and re-evaluate the transfer function $V_o(s)/V_i(s)$ What, if any, is the deviation from the intended design in (c).
 - How would you change the design to restore the Q to 10? You *cannot* remove the 1 M Ω resistor which is across the capacitor.
 - Simulate (i) the circuit in Fig. 2, (ii) the circuit with the inductor replaced by the active inductor², and (iii) the repaired circuit from (e).

²use the circuit with transconductors and capacitors, not the equivalent obtained in (b); Include the 1 M Ω resistor across the

Submit the magnitude and the phase responses;
overlay the responses of the three circuits.