 


EE316: Analog Systems in VLSI: HW1 Solutions


(neglecta kristemporal)



$$V_{out} = V_1 - V_2 = V_T \ln \frac{I_0}{I_s \cdot 100x} - V_T \ln \frac{I_0}{I_s \cdot 272x}$$


$$= V_T \ln \left(\frac{272}{100} \right) \approx \frac{V_T}{1} = 26mV$$

2. (a) Neglect g_{ds} .

 


$$\frac{v_{out}}{v_{in}} = - \frac{g_{m1}}{g_{m2}} = - \frac{\sqrt{I_{bias} \mu C_{ox} \frac{W_1}{L_1}}}{\sqrt{I_{bias} \mu C_{ox} \frac{W_2}{L_2}}}$$

$$= -2$$

 

$$\frac{v_{out}}{v_{in}} = - \frac{g_{m1}}{g_{m2} + g_{mb2}} = -\alpha, \alpha < 2$$


gain reduces

 

$$\frac{v_o}{v_d} = - \frac{\omega_u}{s}, \omega_u = 2\pi \cdot 3 \cdot 10^6 \text{ rad/s}$$

$$\frac{v_o}{v_i} = - \frac{R_1}{R_2} \cdot \frac{1}{1 + \frac{s}{\omega_u} \cdot \frac{R_1 + R_2}{R_2}} = - \frac{2}{1 + s \cdot \tau}$$

$$\tau = \frac{1}{2\pi} \mu s$$

 

2

4 (11.1) $V_{max} = 2^N - 1 \cdot V_{LSB} = 1.023V$

(11.2) $V_{LSB} = \frac{V_{ref}}{2^N} = \frac{3V}{2^{12}}$

Quantization noise rms = $\frac{V_{LSB}}{\sqrt{12}}$

$\frac{1}{2}$ Input rms = $\frac{V_{i,ff}}{2\sqrt{2}}$

$\therefore SNR = \frac{\frac{1}{2\sqrt{2}}}{\frac{3V}{2^{12}} \cdot \frac{1}{2\sqrt{3}}} = \sqrt{\frac{3}{2}} \cdot \frac{1}{3} \cdot 2^{12} \approx 64.5dB$

For 0 dB SNR, $V_{i,rms} = \frac{V_{LSB}}{\sqrt{12}} \Rightarrow V_{i,ff} = 2\sqrt{2} \cdot \frac{V_{LSB}}{\sqrt{12}}$
 $= \sqrt{\frac{2}{3}} \cdot \frac{3V}{2^{12}} V = 0.6mV$

(11.7) offset error = $V_{out} \Big|_{V_{in}=0} = \frac{-0.01V}{V_{LSB}} = -0.01LSB$
 $\left[V_{LSB} = \frac{8V}{2^3} = 1V \right]$

Gain = $\frac{7.08 - (-0.01)}{1} = 7.09$

Gain error = 0.09 $(7.09 - (2^3 - 1))$

Max DNL = ~~$\frac{7.08 - 6.00}{(7.09 - 7.0) \cdot 2}$~~ = 0.072LSB

Max INL = ~~$\frac{0.09}{(7.09 - 7.0)}$~~ - 0.09LSB

See page 3
 [After gain & offset correction, $V'_o[k] = \frac{V_o[k] + 0.01}{7.09/7.0}$, Compute DNL, INL]

(11.8) Max_{abs} error = 0.08V (7.08 - 7.0)
 $= 0.08LSB \approx 6.6$ bits

Max INL = $\log_2 \frac{2^{36} \cdot 1LSB}{0.09LSB} = 6.47$ bits.

$\left[N_{bits} = \log_2 \frac{V_{ref}}{V_{err}} = \log_2 \frac{2^{N_{ideal}} V_{LSB,ideal}}{V_{err}} \right]$

(11.10)

	Actual	Ideal	
00	0.01V	0V	$V_{LSB} = 1V$
01	1.02V	1V	offset = $\frac{0.01V}{1V} = 0.01LSB$
10	1.97V	2V	
11	3.02V	3V	Gain = $\frac{3.02V - 0.01V}{1V \cdot (2^2 - 1)} = 3.01$

Gain error = $3.01 - 3 = 0.01LSB$

Worst case absolute error = $-0.03V \equiv -0.03LSB$

(11.12) For ΔV (due to jitter) to be less than $1V_{LSB}$,

$$\Delta t < \frac{1}{2^N \pi f_{in,max}} = 2.43 \times 10^{-10} s = 243ps$$

Characteristics of the D/A converter in 11.7

given : -0.01^* , 1.02^* , 2.02 , 2.96 , 3.95 , 5.02 , 6 , 7.08^{**} (*: offset)

remove offset : 0 , 1.04 , 2.03 , 2.97 , 3.96 , 5.03 , 6.01 , 7.09^{\dagger} (\dagger : gain)

(+0.01)

remove gain error : 0 , 1.027 , 2.004 , 2.932 , 3.910 , 4.966 , 5.934 , 7.0

($\times \frac{7.0}{7.09}$)

INL : 0 , 0.027 , 0.004 , -0.068 , 0.090^{\ddagger} , 0.034 , 0.066 , 0 (\ddagger : max INL)

DNL : -0.027 , -0.023 , -0.072^* , -0.023 , 0.056 , -0.032 , 0.066

($*$: Max DNL)