

E 4316: Analog systems in VLSI



HN3 solutions Wagendra Krishnapura

1) (12.7) Worst case DNL occurs @ MSB transition

	Ideal	Actual
0111 1111	127C	$127C(1-0.005) = 126.365$
1000 0000	128C	$128C(1+0.005) = 128.64$
step	C	2.275C
DNL =	$\frac{2.275C - C}{C} = \underline{1.275 \text{ LSB}}$	

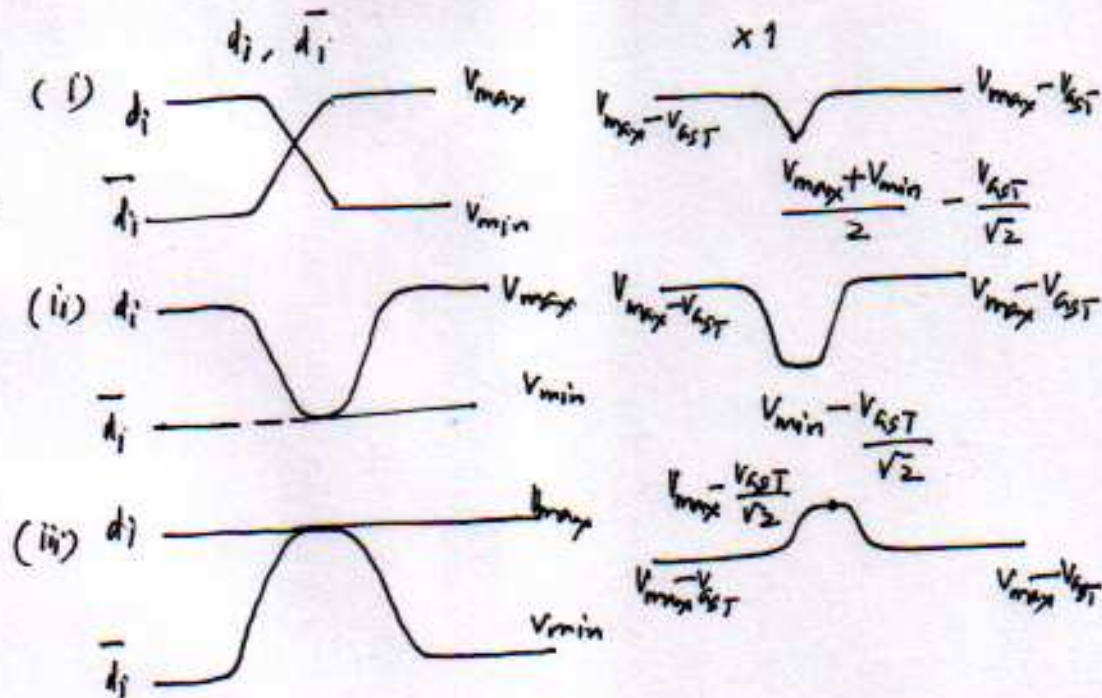 
(12.8)

Define  $V_{AST} = V_{GS}(Q_1) - V_T$  when  $I_D(Q_1) = I_0$   
 (also =  $V_{GS}(Q_2) - V_T$  when  $I_D(Q_2) = I_0$ )



The jump in  $v_{out}$  increases if  $d_i, \bar{d}_i$  don't cross at the midpoint of  $V_{max}, V_{min}$

(12.16)

 


approx. behavior

$V_{d_i} < V_{bias}$ :  $Q_1$  acts as a source follower


$V_{d_i} > V_{bias}$ :  $Q_2$  acts as a source follower.

The problem says "threshold voltage", but the gate-source drop is  $|V_{gs}| = V_T + ()$ .

 Assume that  $V_{gs}(Q_1) = -1.5V @ I_{ds}(Q_1) = -I_0$



(12.18)

 

$$50 \mu A = \frac{92 \mu A / V^2}{2} \cdot \frac{W}{L} (3V - 1V)^2$$


$$\therefore \frac{W}{L} = 0.272$$

$$g_m = 92 \mu A / V^2 \cdot \frac{W}{L} (3V - 1V) = 50 \mu S$$

$$\Delta V = 1mV \Rightarrow \Delta I = 50nA$$

$$\frac{\Delta I}{I} = \frac{50nA}{50 \mu A} = 0.1\%$$

(12.17)

 

$$5 \mu A = \frac{92 \mu A / V^2}{2} \cdot \frac{W}{L} (3V - 1V)^2$$

$$\therefore \frac{W}{L} = 0.0272$$

$$g_m = 92 \mu A / V^2 \cdot \frac{W}{L} (3V - 1V) = 5 \mu S$$

$$\Delta V = 1mV \Rightarrow \Delta I = 5nA$$

$$\frac{\Delta I}{I} = \frac{5nA}{5 \mu A} = 0.1\% \cdot \frac{\Delta I}{I_{ref}} = 0.01\%$$



12.17, 12.18:

$$\frac{\Delta I}{I_0} = \frac{g_m \cdot \Delta V}{I_0}$$

$$= \frac{\mu_{ox} \frac{W}{L} \cdot (V_{GS} - V_T)}{\frac{\mu_{ox} \frac{W}{L} (V_{GS} - V_T)^2}{2}} \cdot \Delta V$$

∴ % change in the transistor current is a function of only  $(V_{GS} - V_T)$ . It is the same for the 2 cases.

2). (a).

10 bit dac.


$$I_{unit} = \frac{\Delta V_{out, max} / R}{2^N - 1} = \frac{1.023V / 200\Omega}{1023} = 5\mu A$$

(b)  $V_{out, min} = V_{dd} - 1.023V = 1.477V$

$V_g - V_{out, min} \leq V_T$  to keep  $M_3$  in saturation

∴  $V_g \leq 2.227V$

(c)

 

When  $M_2$  just turns off,

$V_{bi} = V_L$

$V_{GS, M_2} = V_T ; V_{GS, M_3} = V_T + \sqrt{I_{unit} \frac{2L}{\mu_{ox} W}}$



∴  $V_{bi} = V_g + \sqrt{I_{unit} \frac{2L}{\mu_{ox} W}}$

$V_L = 1.75V + 0.141V = 1.891V$

|||y

$V_H = 2.227V + 0.141V = 2.368V$

(d). Lowest voltage on  $M_1$  drain when  $M_2$  is OFF

$$V_{d,M_1} = V_g - V_{gs,M_1} = V_g - V_T - \sqrt{I_{unit} \frac{2L}{\mu C_{ox} W}}$$

$$= 1.336V$$

$$V_{bias} - V_{d,M_1} \leq V_T$$

$$\therefore V_{bias} \leq 2.086V$$

(e)  $\frac{W}{L} = 0.056$

(f) current mismatch between 2 current sources =  $\Delta V_T \cdot g_m = DNL \cdot I_{unit}$

$$g_m = \mu C_{ox} \frac{W}{L} (V_{gs} - V_T) = 7.49 \mu S$$



given:  $g_m \cdot \sigma_{V_T} \leq \frac{I_{LSB}}{4} = 1.25 \mu A$

$$\sigma_{V_T} \leq \frac{1.25 \mu A}{7.49 \mu S} = 167 mV$$

N&L can be computed, but at the 10 bit level, the ~~desired~~ mismatch is so large that it makes no sense for the DNL specification. a variable

(gate area  $\approx 0.101 \mu^2$ ).

If INL is required to be  $\leq \frac{1}{4} LSB$ ,

$$INL [n] \approx \frac{n}{N} \sqrt{N-n} \cdot \frac{\sigma(\Delta I) / \sqrt{2}}{I_{unit}}$$

$$INL_{max} \text{ (at } n = N/2) = \frac{1}{2} \sqrt{\frac{N}{2}} \cdot \frac{\sigma(\Delta I) / \sqrt{2}}{I_{unit}} \leq \frac{1}{4} LSB$$


$$\sigma(\Delta I) = 0.156 \mu A$$



$$\sigma_{V_T} \leq \frac{0.156 \mu A}{7.49 \mu S} = 20.8 mV$$

$WL = 0.058 \mu m^2$ , still very small.

(g)

 

Assuming ~~0.25 μm~~<sup>0.5</sup> devices for both  $M_3$  &  $M_1$ ,


$$\lambda = \frac{0.2 V^{-1}}{0.85} = \cancel{0.235} \cdot 0.4 V^{-1}$$

$$\text{output resistance } r_{ds} = \frac{1}{\lambda I_D} = \cancel{500 k\Omega} \cdot 500 k\Omega$$

$$g_{m3} = \mu C_{ox} \frac{W}{L} (V_{gs} - V_T) = 70.7 \mu S$$

$$r_{out, cell} = g_{m3} r_{ds3} r_{ds1} + r_{ds1} + r_{ds3} = 18.7 M\Omega$$

 (h). Absolute error of  $\frac{1}{2}$  LSB



$$\begin{aligned} \text{Error} &= |I_{max} \cdot (R_L \parallel R_{out}) - I_{max} \cdot R_L| \\ &= I_{max} \cdot \frac{R_L^2}{R_L + R_{out}} = \frac{I_{unit} \cdot R_L}{2} \leftarrow V_{LSB} \end{aligned}$$

$$\therefore R_{out} = \frac{2 R_L^2}{I_{unit} / I_{max}} - R_L$$

$$= (2(2^N - 1) - 1) R_L$$

$$\therefore R_{out} = 409 k\Omega$$

$$R_{out} = \frac{R_{out, cell}}{2^N - 1}$$

$$\begin{aligned} \therefore R_{out, cell} &= R_{out} \cdot 2^N - 1 \\ &= \underline{418 M\Omega} \end{aligned}$$

(parallel connection)

[The ~~re~~ output resistance computed in (g) is insufficient.  
A longer channel needs to be used for  $M_1$ .]

(i)  $1\text{fF}/\mu\text{m}$  capacitance for  $M_3$

$$\therefore \text{total capacitance} = 2.5\mu\text{m} \cdot \frac{1\text{fF}}{\mu\text{m}} \cdot 1023 = 2.56\text{pF}$$

Setting to  $\frac{1}{2}$  LSB  $\left( = \frac{1}{2^{11}} \right) =$

$$e^{-T_{\text{settle}}/\tau} = \frac{1}{2^{11}}$$

$$T_{\text{settle}} = \tau \cdot 11 \cdot \ln(2) = RC \cdot 11 \cdot \ln(2) \approx 3.9\text{ns}$$

$$\therefore \text{conversion rate} = \frac{1}{3.9\text{ns}} = 256\text{MHz}$$