

E6316: Analog systems in VLSI, Fall 2004

HW4 Solutions: Nagendra Krishnapura

1. (a) m^{th} transition of A/D 1 when

$$V_{in} + V_{es/H} = V_{e, A/D1} [m] + m V_{LSB}$$

$$V_{in} = V_{e, A/D1} [m] + m V_{LSB} - V_{es/H}$$

(b) D/A output = $m \cdot V_{LSB1} + V_{e, D/A} [m]$

k^{th} transition of A/D 2 when

$$\left[V_{in} + V_{es/H} - (m V_{LSB1} + V_{e, D/A} [m]) \right] G + V_{e, amp} = m k V_{LSB2} + V_{e, A/D2} [k]$$

$$V_{in} = m V_{LSB1} + \frac{k V_{LSB2}}{G} + V_{e, D/A} [m] - V_{es/H} - \frac{V_{e, amp}}{G} + \frac{V_{e, A/D2} [k]}{G}$$

(c) From (a): $V_{in} = m V_{LSB} + V_{e, A/D1} [m] - V_{es/H}$

$$\therefore |V_{e, A/D1} [m]| + |V_{es/H}| \leq \frac{V_{LSB}}{2} = \frac{V_{ref}}{2^{M+K+1}} = \frac{V_{ref}}{2^{N+1}}$$

Equal contributions:

$$|V_{e, A/D1} [m]| \leq \frac{V_{ref}}{2^{N+2}} ; |V_{es/H}| \leq \frac{V_{ref}}{2^{N+2}}$$

(d) From (b):

$$\text{Error} = |V_{e, D/A} [m]| + |V_{es/H}| + \left| \frac{V_{e, amp}}{G} \right| + \left| \frac{V_{e, A/D2} [k]}{G} \right| \leq \frac{V_{ref}}{2^{N+1}}$$

Equal contributions:

$$|V_{eD/A} [m]| \leq \frac{1}{4} \cdot \frac{V_{ref}}{2^{N+1}} = \frac{V_{ref}}{2^{N+3}} \quad [N+2 \text{ bit accuracy}]$$

$$* |V_{eS/H}| \leq \frac{1}{4} \frac{V_{ref}}{2^{N+1}} = \frac{V_{ref}}{2^{N+3}} \quad [N+2 \text{ bit accuracy}]$$

$$\left| \frac{V_{eamp}}{G} \right| \leq \frac{1}{4} \frac{V_{ref}}{2^{N+1}} \quad \therefore |V_{eamp}| \leq \frac{2^M V_{ref}}{2^{N+3}}$$

$$\{G = 2^M\} \quad = \frac{V_{ref}}{2^{K+3}}$$

$$\left| \frac{V_{eA/D_2} [k]}{G} \right| \leq \frac{1}{4} \frac{V_{ref}}{2^{N+1}} \quad \therefore |V_{eA/D_2} [k]| \leq \frac{V_{ref}}{2^{K+3}}$$

strictly condition than
in (a)

$K+2$ bit accuracy.

② $M=5, K=3$

A/D #1: $N+1$ bit accuracy = 9 bit accuracy

S/H : $N+2$ bit accuracy = 10 bit accuracy

D/A : " = 10 bit accuracy

~~V_{eamp}~~ amplifier : $K+2$ bit accuracy = 5 bit accuracy

A/D₂ : $K+2$ bit accuracy = 5 bit accuracy


Similarly for $M=4, K=4$

A/D #1: 9 bits, S/H & D/A : 10 bits

amplifier and A/D #2 : 6 bits.

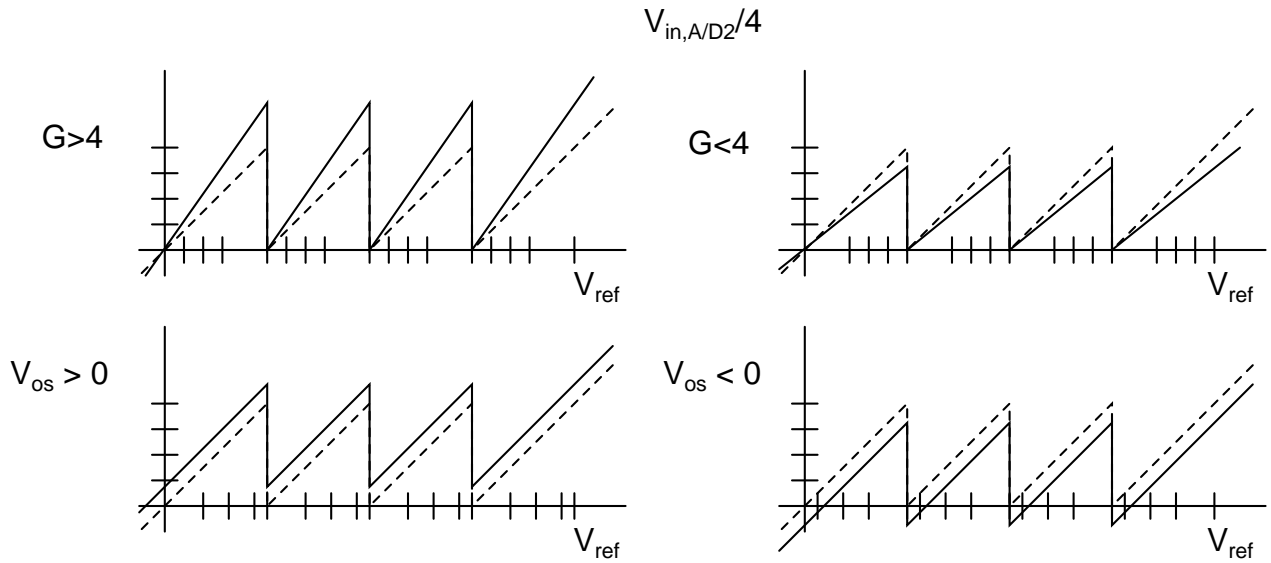
Problem #2: The 2nd A/D quantizes the amplified residue

$V_{in,A/D2}$: The input to the second A/D converter



dashed: ideal, solid: actual

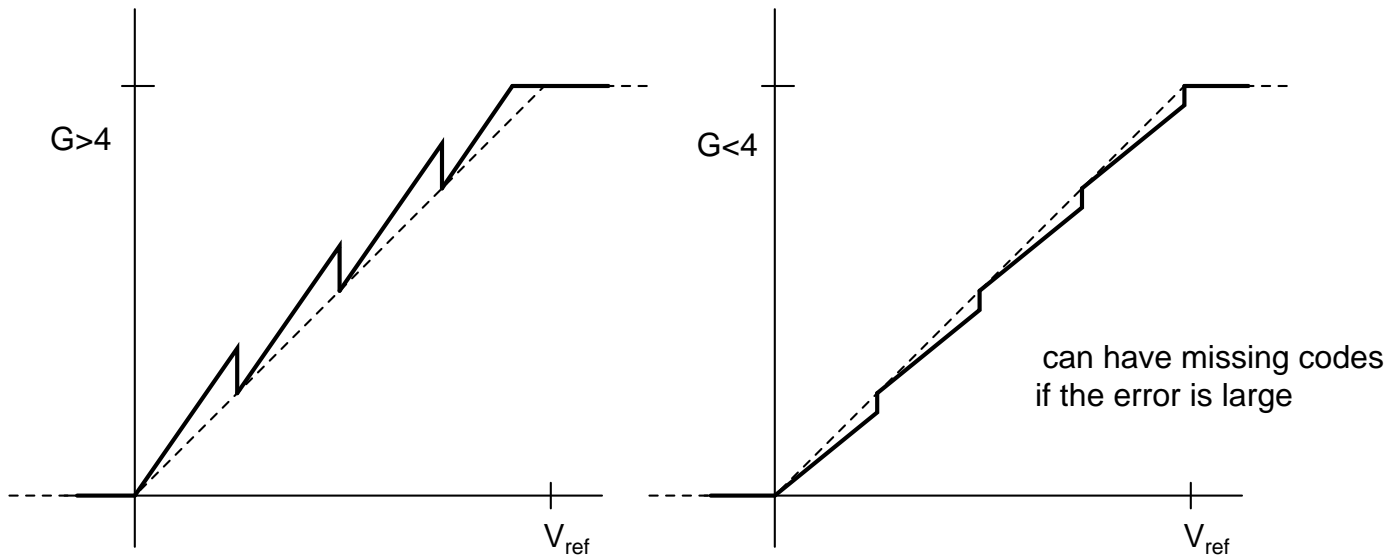X axis markings show the decision levels.



A/D characteristics shown as a transfer curve (straight line passing through the steps)

They can be similarly generated for the case with offsets